

RAJSHAHI UNIVERSITY OF ENGINEERING AND TECHNOLOGY
LAB REPORT - 03

COURSE NAME: SESSIONAL BASED ON CSE 2103
COURSE CODE: CSE 2104

SUBMITTED TO-

Prof. Dr. Boshir Ahmed

Professor

Department of Computer Science & Engineering
Rajshahi University of Engineering & Technology

Md. Zahirul Islam

Lecturer

Department of Computer Science & Engineering
Rajshahi University of Engineering & Technology

SUBMITTED BY-

Srabonti Deb

Roll-1803163

Section - C

Department of Computer Science & Engineering

SUBMISSION DATE -17 MARCH, 2021

4.1) Experiment Name: Implement Various Logic Functions (For Example $F(a, b, c, d) = \text{SOP}(0, 2, 3, 4, 6, 10, 14, 15)$).

Objectives:

- To learn about Boolean algebra.
- To understand what are combinational logic circuits.
- To learn about canonical & standard form.
- To learn about using the sum-of-products method to design a logic circuit based on a design truth table.
- To learn about how to simplify Boolean expression.
- To learn about maxterm & minterm & how to find out these.

Theory: Digital circuit operates using digital signals. These signals have discrete binary values: zero and one. Zero signifies the false state while one signifies the true state. Boolean algebra is a type of algebra that helps to represent binary numbers and binary variables. Canonical form is a method of representing Boolean functions of Boolean algebra while standard form is a simplified version of canonical form.

Minterm: A product term in which all the variables appear exactly once, either complemented or uncomplemented. Denoted by m_j , where j is the decimal equivalent of the minterm's corresponding binary combination (b_j).

Maxterm: A sum term in which all the variables appear exactly once, either complemented or uncomplemented. Denoted by M_j , where j is the decimal equivalent of the maxterm's corresponding binary combination (b_j).


Truth Table notation for Minterms and Maxterms:

x	y	z		Minterm	Maxterm
0	0	0		$x'y'z' = m_0$	$x+y+z = M_0$
0	0	1		$x'y'z = m_1$	$x+y+z' = M_1$
0	1	0		$x'yz' = m_2$	$x+y'+z = M_2$
0	1	1		$x'yz = m_3$	$x+y'+z' = M_3$
1	0	0		$xy'z' = m_4$	$x'+y+z = M_4$
1	0	1		$xy'z = m_5$	$x'+y+z' = M_5$
1	1	0		$xyz' = m_6$	$x'+y'+z = M_6$
1	1	1		$xyz = m_7$	$x'+y'+z' = M_7$

Experimental Analysis:


- **Circuit Diagram:**

4.1.1- Drag & drop circuit diagram:

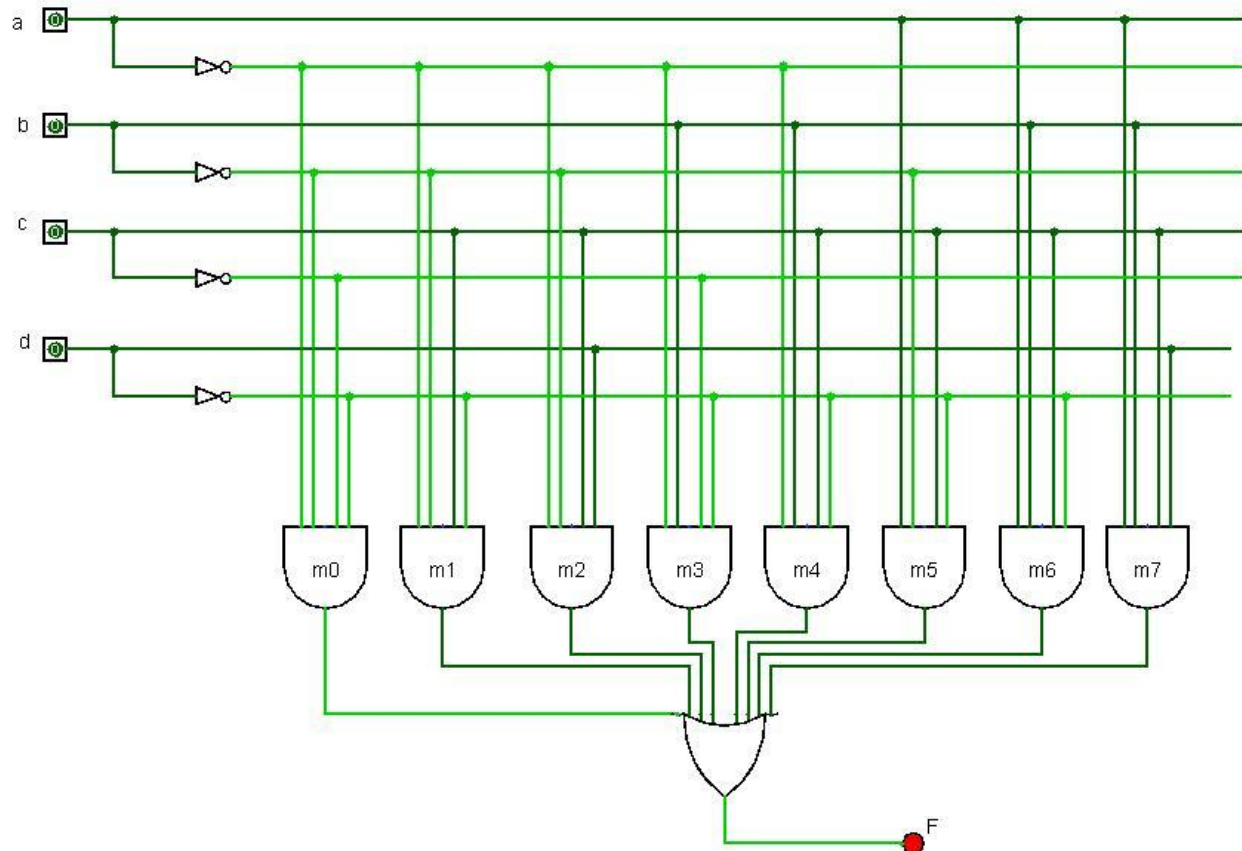

4.1.1-(Drag & drop) Implement Various Logic functions (For example $F(a,b,c,d) = \text{SOP}(0,2,3,4,6,10,14,15)$)

4.1.2-Analyse circuit diagram:

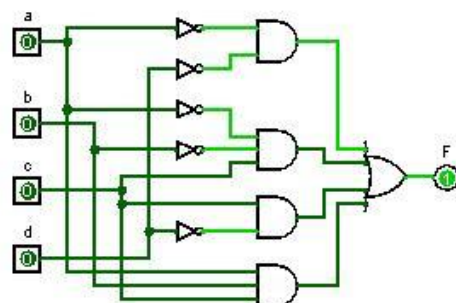

4.1.2-(Analyse) Implement Various Logic functions (For example $F(a,b,c,d) = \text{SOP}(0,2,3,4,6,10,14,15)$)

- **Truth Table:**

a	b	c	d	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Conclusion: In this experiment, we discussed about canonical form, its characteristics and diagram.

4.2) Experiment Name: Verify the result of simplified version of F in 1.

Objectives:

- To learn about how to simplify Boolean expression.
- To learn about how to use rules of Boolean expression.


Theory: In Boolean algebra simplification, a Boolean expression is translated to another form with less number of terms and operations.

Handwritten simplification of a Boolean expression:

$$\begin{aligned} \text{Simplification: } & \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}b\bar{c}d + \bar{a}bcd \\ & + \bar{a}b\bar{c}\bar{d} + \bar{a}bc\bar{d} + \bar{a}bcd + abcd \\ \Rightarrow & \bar{a}\bar{b}\bar{d} + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}bc\bar{d} + \bar{a}bcd \\ & + abcd \quad [\because c + \bar{c} = 1] \\ \Rightarrow & \bar{a}\bar{d}(\bar{b} + bc) + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}bc\bar{d} \\ & + abcd + abcd. \\ \Rightarrow & \bar{a}\bar{d}(\bar{b} + c) + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}bc\bar{d} \\ & + abcd + abcd \\ \Rightarrow & \bar{a}\bar{d}(\bar{b} + c + b\bar{c}) + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}bc\bar{d} + abcd \\ \Rightarrow & \bar{a}\bar{d}\{(\bar{b} + c + b)(\bar{b} + c + \bar{c})\} + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} \\ & + \bar{a}bc\bar{d} + abcd. \\ \Rightarrow & \bar{a}\bar{d} + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}bc(d + \bar{d}) \\ \Rightarrow & \bar{a}\bar{d} + \bar{a}\bar{b}cd + \bar{a}b\bar{c}\bar{d} + \bar{a}bc \\ \Rightarrow & \bar{a}\bar{d} + \bar{a}\bar{b}cd + \bar{a}c(b + b\bar{d}) \\ \Rightarrow & \bar{a}\bar{d} + \bar{a}\bar{b}cd + \bar{a}c\bar{d} + \bar{a}bc. \\ \Rightarrow & \bar{d}(\bar{a} + \bar{a}c) + \bar{a}\bar{b}cd + \bar{a}bc \\ \Rightarrow & \bar{d}(\bar{a} + c) + \bar{a}\bar{b}cd + \bar{a}bc \\ \Rightarrow & \bar{a}\bar{d} + c\bar{d} + \bar{a}\bar{b}cd + \bar{a}bc. \\ \Rightarrow & \bar{a}\bar{d} + c\bar{d} + \bar{a}(\bar{d} + \bar{a}\bar{b})(\bar{d} + d) + \bar{a}bc \\ \Rightarrow & \bar{a}\bar{d} + c\bar{d} + \bar{a}\bar{b}c + \bar{a}bc \\ \Rightarrow & \bar{a}\bar{d} + c\bar{d} + \bar{a}b\bar{c} + \bar{a}bc \end{aligned}$$

Experimental Analysis:

- **Circuit Diagram:**

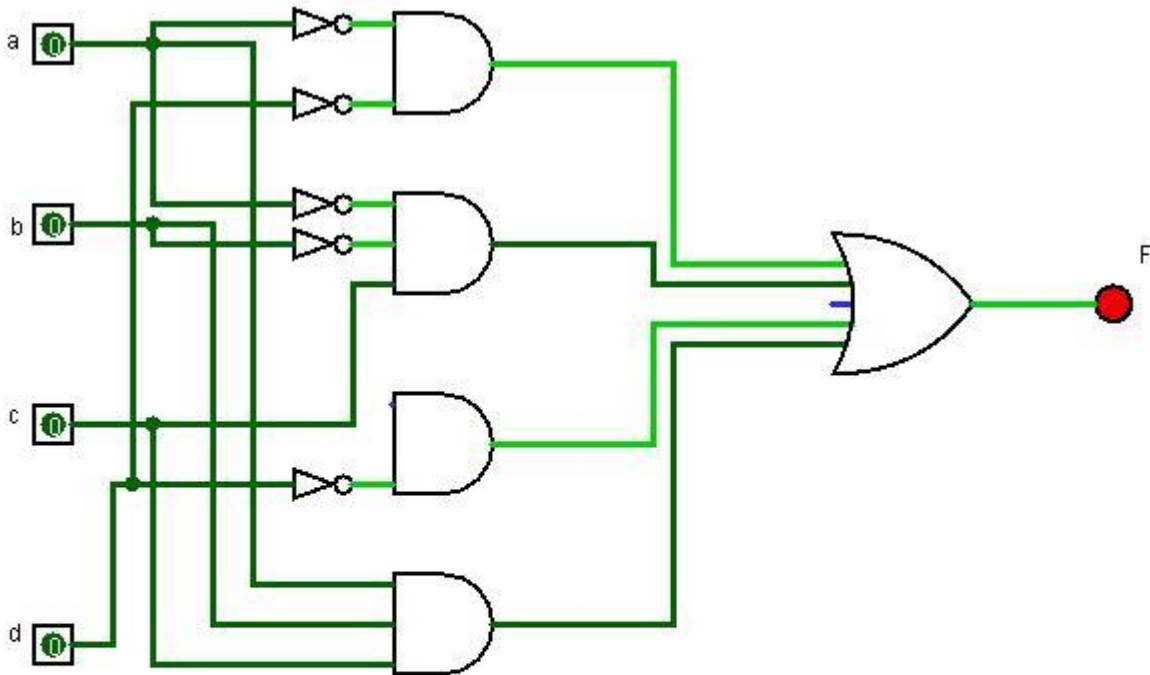

4.2-Verify the result of simplified version of F in 1.

- **Truth Table:**

a	b	c	d	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

Conclusion: We can say that the result of simplified version of F in 1 is verified.