

RAJSHAHI UNIVERSITY OF ENGINEERING AND TECHNOLOGY
LAB REPORT - 04

COURSE NAME: SESSIONAL BASED ON CSE 2103
COURSE CODE: CSE 2104

SUBMITTED TO-

Prof. Dr. Boshir Ahmed

Professor

Department of Computer Science & Engineering
Rajshahi University of Engineering & Technology

Md. Zahirul Islam

Lecturer

Department of Computer Science & Engineering
Rajshahi University of Engineering & Technology

SUBMITTED BY-

Srabonti Deb

Roll-1803163

Section - C

Department of Computer Science & Engineering

SUBMISSION DATE -3 JULY,2021

5.1) Experiment Name: Verify the Half Adder Circuit.

Objectives:

- To learn the properties of Half Adder Circuit.
- To know the different implementation ways of Half Adder Circuit.
- To draw the diagram of Half Adder Circuit.
- To write the Boolean expression for Half Adder Circuit.
- To generate the truth table of a Half Adder Circuit.

Theory: A combinational circuit that performs the addition of two bits is called a Half Adder Circuit. The Half Adder is able to add two single binary digits and provide the output plus a carry value. It has two inputs x and y, and two outputs S (sum) and C (carry). The common representation uses a XOR gate and an AND gate.

Using basic gates:

$$S = x \oplus y + xy$$

$$C = xy$$

Using the universal gates:


$$S = x \oplus y$$

$$C = xy$$

Experimental Analysis:


- **Circuit Diagram:**

 5.1.1- The Half Adder Circuit(Using Basic Gates)



5.1.1 The Half Adder Circuit(using the basic gates)

 5.1.2- The Half Adder Circuit(Using Universal Gates)



5.1.2 The Half Adder Circuit(using the universal gates)

- Truth Table:**

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Conclusion: In this experiment, we discussed about Half Adder Circuit using both basic gates and universal gates. The truth table shows the exact result in both ways of implementation.

5.2) Experiment Name: Verify the Full Adder Circuit.

Objectives:

- To learn the properties of Full Adder Circuit.
- To know the different implementation ways of Full Adder Circuit.
- To draw the diagram of Full Adder Circuit.
- To write the Boolean expression for Full Adder Circuit.
- To generate the truth table of a Full Adder Circuit.

Theory: A combinational circuit that is able to add three single binary digits and provide the output and a carry value is called a Full Adder Circuit. It has three inputs x,y and z, and two outputs S (sum) and C (carry). The common representation uses three AND gate, an OR gate and a XOR gate.

Using basic gates:

$$S = x^{\wedge}y^{\wedge}z + x^{\wedge}yz^{\wedge} + xy^{\wedge}z^{\wedge} + xyz$$

$$C = xy + xz + yz$$

Using the universal gates:


$$S = (x \oplus y) \oplus z$$

$$C = xy + yz + zx$$

Experimental Analysis:


- **Circuit Diagram:**

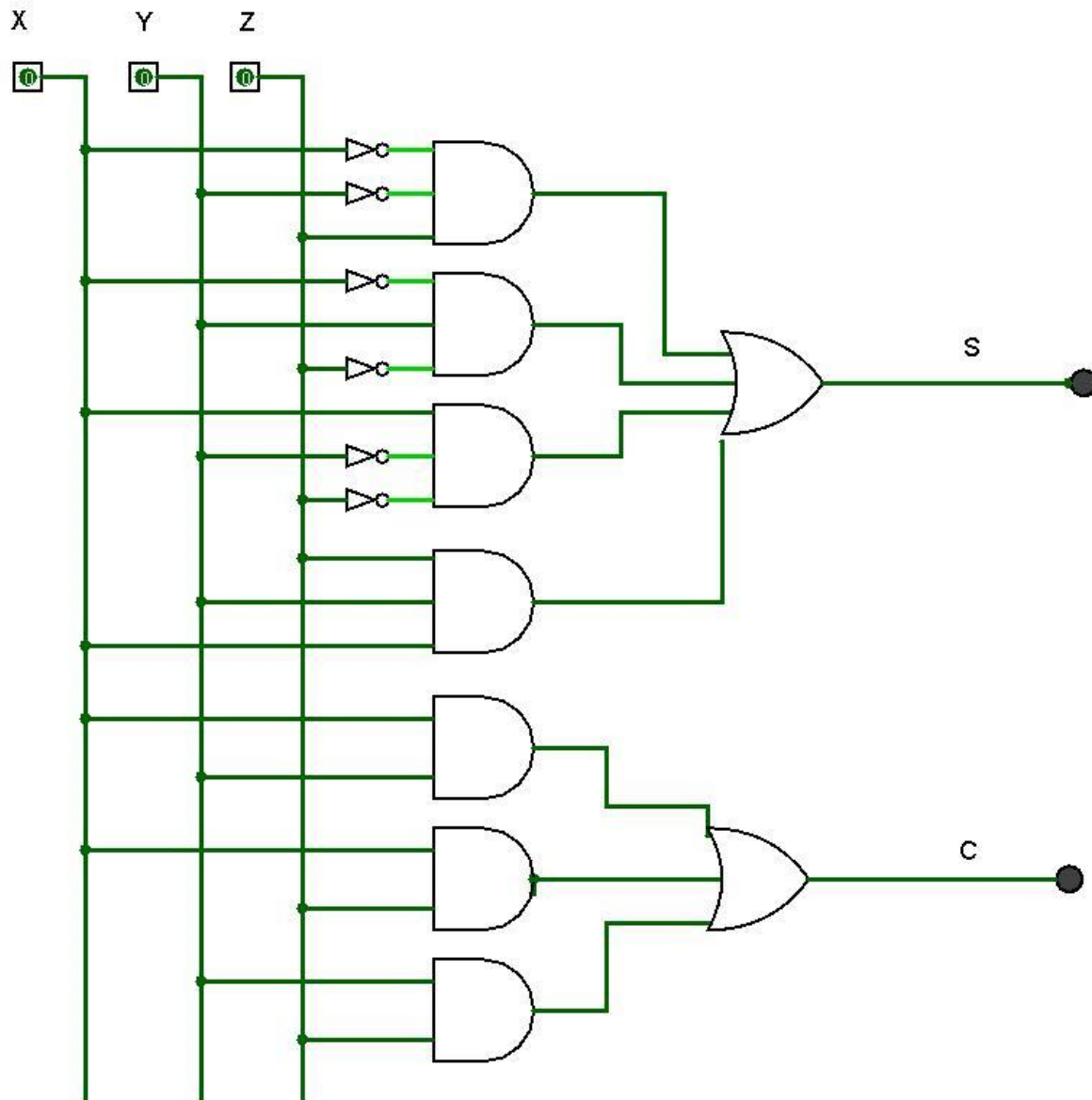5.2.1- The Full Adder Circuit(Using Basic Gates)



5.2.1 The Full Adder Circuit(using the basic gates)

 5.1.2- The Full Adder Circuit(Using Universal Gates)



5.2.2 The Full Adder Circuit(using the universal gates)

- **Truth Table:**

X	Y	Z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Conclusion: In this experiment, we discussed about Full Adder Circuit using both basic gates and universal gates. The truth table shows the exact result in both ways of implementation.

5.3) Experiment Name: Implement the Full Adder Circuit by using Half Adder Circuit and verify the result.

Objectives:

- To draw the diagram of Full Adder Circuit using Half Adder Circuit.
- To generate the truth table of a Full Adder Circuit.
- To verify the result of the implementation.

Theory: A combinational circuit that is able to add three single binary digits and provide the output and a carry value is called a Full Adder Circuit. It has three inputs x,y and z, and two outputs S (sum) and C (carry). The common representation uses three AND gate, an OR gate and an XOR gate.

Using basic gates:

$$S = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

Using the universal gates:

$$S = (x \oplus y) \oplus z$$


$$C = xy + yz + zx$$

A Full Adder Circuit can be represented using two Half Adder Circuits and an OR gate.

Experimental Analysis:

- **Circuit Diagram:**

 5.3- The Full Adder Circuit Using Half Adder Circuit



5.3 The Full Adder Circuit by Using Half Adder

Truth Table:

X	Y	Z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Conclusion: In this experiment, we discussed about Full Adder Circuit using Half Adder Circuit. The truth table shows the exact result of implementation.