

**RAJSHAHI UNIVERSITY OF ENGINEERING AND TECHNOLOGY**  
**LAB REPORT - 02**

COURSE NAME: SESSIONAL BASED ON CSE 2103  
COURSE CODE: CSE 2104

**SUBMITTED TO-**

**Prof. Dr. Boshir Ahmed**

Professor

Department of Computer Science & Engineering  
Rajshahi University of Engineering & Technology

**Md. Zahirul Islam**

Lecturer

Department of Computer Science & Engineering  
Rajshahi University of Engineering & Technology

**SUBMITTED BY-**

Srabonti Deb

Roll-1803163

Section - C

Department of Computer Science & Engineering

SUBMISSION DATE -11 MARCH, 2021

**3.1) Experiment Name:** Verify the Basic NOR gate (up to 5 Inputs) for all input combinations.

**Objectives:**


- To study and understand the NOR gate.
- To implement the logic circuit operation using NOT & OR gate.
- To write the Boolean expression for NOR gate.
- To draw the diagram of NOR gate.
- To generate the truth-table of NOR gate.

**Theory:** The circuit which produces an output signal only when there are no signals on any of the input connections is called **NOR** gate. The output of a NOR gate is true if all of its inputs are false or zero. On the other hand, If one or more of the inputs are true, then the output is false. Suppose Z is output and A, B are two inputs then we express the NOR gate as:  $Z = \overline{A + B}$

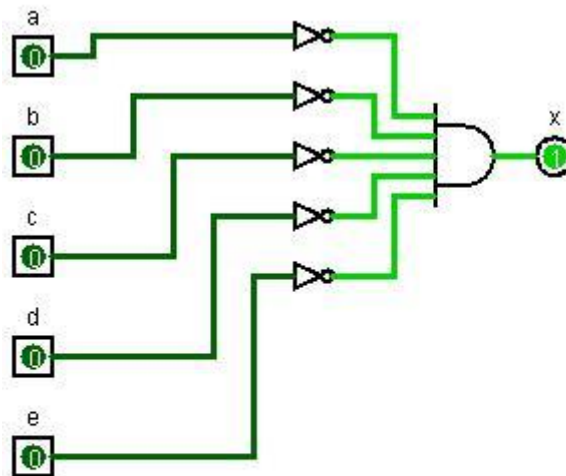**Experimental Analysis:**


- **Circuit Diagram:**

When all the input signals are 0, the output is 1.



Exp: 3.1.2

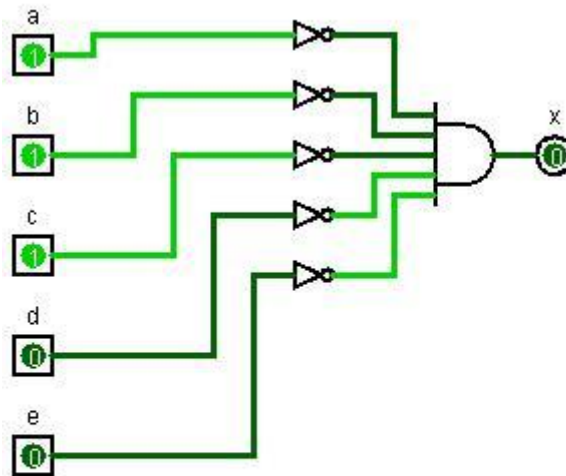On the other hand, when one or more input signals is 1, the output is 0.



Exp: 3.1.2

- **Truth Table:**

a	b	c	d	e	x
0	0	0	0	0	1
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	0
1	0	1	0	0	0
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	0

**Conclusion:** In this experiment, we discussed about NOR gate operation by giving five inputs. From the truth table, we came to know that a high output(1) results if all of the five inputs of the gate are low(0) & if one or more input is high (1), a low output(0) results.

**3.2) Experiment Name:** Verify the Basic NAND gate (up to 5 Inputs) for all input combinations.

**Objectives:**


- To study and understand the NAND gate.
- To implement the logic circuit operation using AND & NOT gate.
- To write the Boolean expression for NAND gate.
- To draw the diagram of NAND gate.
- To generate the truth-table of NAND gate.

**Theory:** A NAND gate is a logic gate which produces an output which is false only if all its inputs are true. Its output is complement to the output of an AND gate. Suppose Z is output and A,B are the two inputs, then we can represent the NAND gate as :  $Z = \overline{AB}$

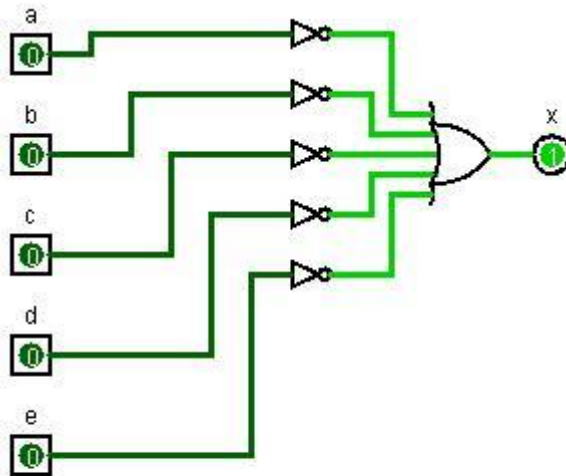**Experimental Analysis:**


- **Circuit Diagram:**

When all the inputs are 0, the output is 1.



Exp: 3.2.2

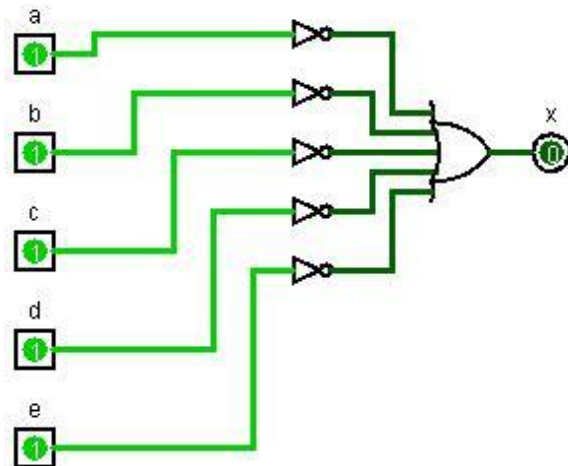When all the inputs are 1, the output is 0.



Exp: 3.2.2

- **Truth Table:**

a	b	c	d	e	x
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	1
0	0	1	0	0	1
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	1
0	1	1	0	0	1
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	1
1	1	1	0	0	1
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	0

**Conclusion:** In this experiment, we discussed about NAND gate operation by giving five inputs. From the truth table, we came to know that a low output results only if all the five inputs of the gate are high and if any input is low, a high output results.

**3.3) Experiment Name:** Verify the Basic X-OR gate for all input combinations.

**Objectives:**

- To study and understand the X-OR gate.
- To implement the logic circuit operation using AND,OR and NOT gate.
- To write the Boolean expression for X-OR gate.
- To draw the diagram of X-OR gate.
- To generate the truth-table of X-OR gate.


**Theory:** X-OR gate is a digital logic gate that gives a true output when the number of true inputs is odd.It is the combination of AND,OR and NOT gate.Suppose Z is output and A,B are the two inputs,then we can represent the X-OR gate as:  **$Z = A\bar{B} + \bar{A}B$**

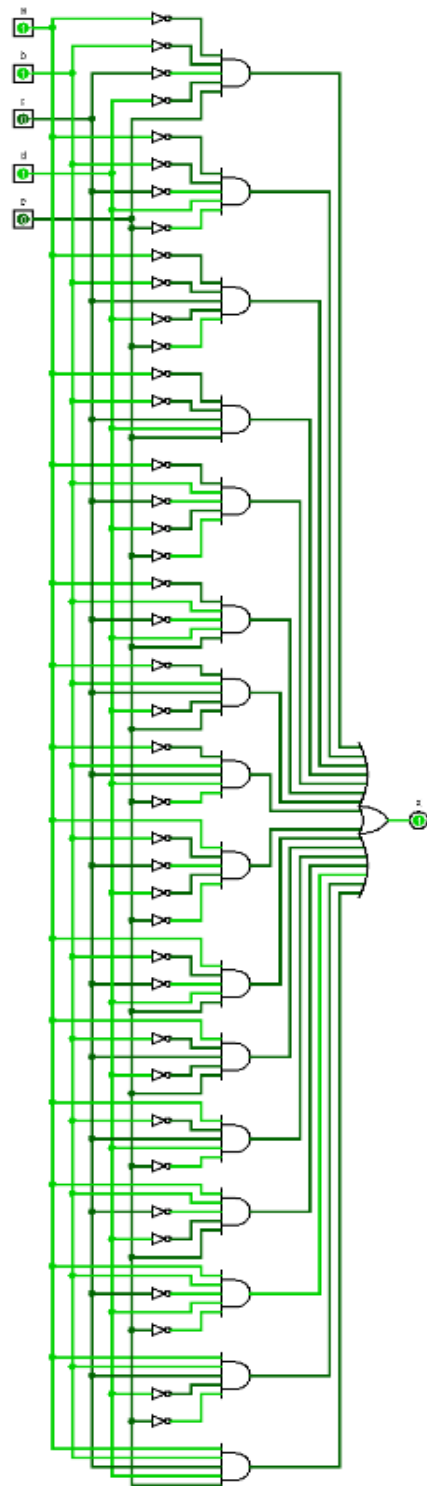**Experimental Analysis:**

- **Circuit Diagram:**




When odd number of inputs are 1, the output is 1.



Exp: 3.3.2

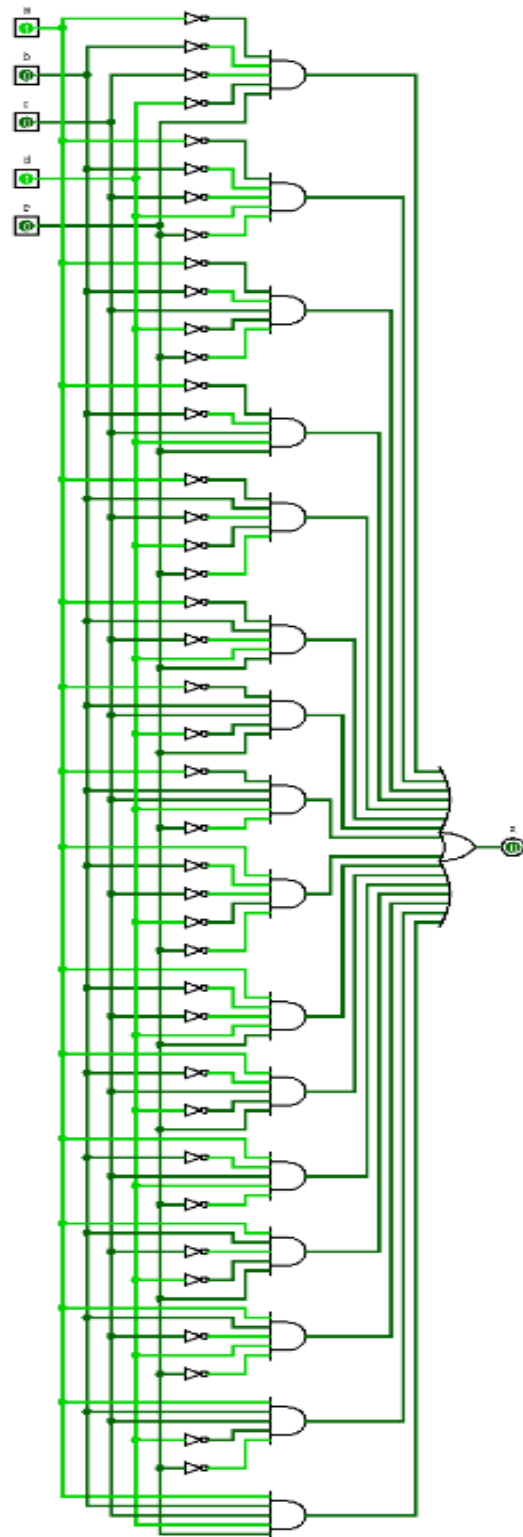When even number of inputs are 1, the output is 0.



Exp: 3.3.2

- **Truth Table:**

a	b	c	d	e	x
0	0	0	0	0	0
0	0	0	0	1	1
0	0	0	1	0	1
0	0	0	1	1	0
0	0	1	0	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	0	1	0
0	1	0	1	0	0
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	0	1	1
0	1	1	1	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	0	1	0
1	0	0	1	0	0
1	0	0	1	1	1
1	0	1	0	0	0
1	0	1	0	1	1
1	0	1	1	0	1
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	0	1	1
1	1	0	1	0	1
1	1	0	1	1	0
1	1	1	0	0	1
1	1	1	0	1	0
1	1	1	1	0	0
1	1	1	1	1	1

**Conclusion:** In this experiment, we discussed about X-OR gate operation by giving five inputs. From the truth table, we came to know that a true output results if odd number of the inputs to the gate is true. On the other hand, if even number of inputs are true, a false output results.

**3.4) Experiment Name:** Verify the Basic X-NOR gate (up to 5 Inputs) for all input combinations.

**Objectives:**


- To study and understand the X-NOR gate.
- To implement the logic circuit operation using AND,OR and NOT gate.
- To write the Boolean expression for X-NOR gate.
- To draw the diagram of X-NOR gate.
- To generate the truth-table of X-NOR gate.

**Theory:** X-NOR gate is a digital logic gate that gives a true output when the number of true inputs is even. It is the combination of AND,OR and NOT gate. Suppose Z is output and A,B are the two inputs, then we can represent the X-OR gate as:  $Z = \sim(A\bar{B} + \bar{A}B)$

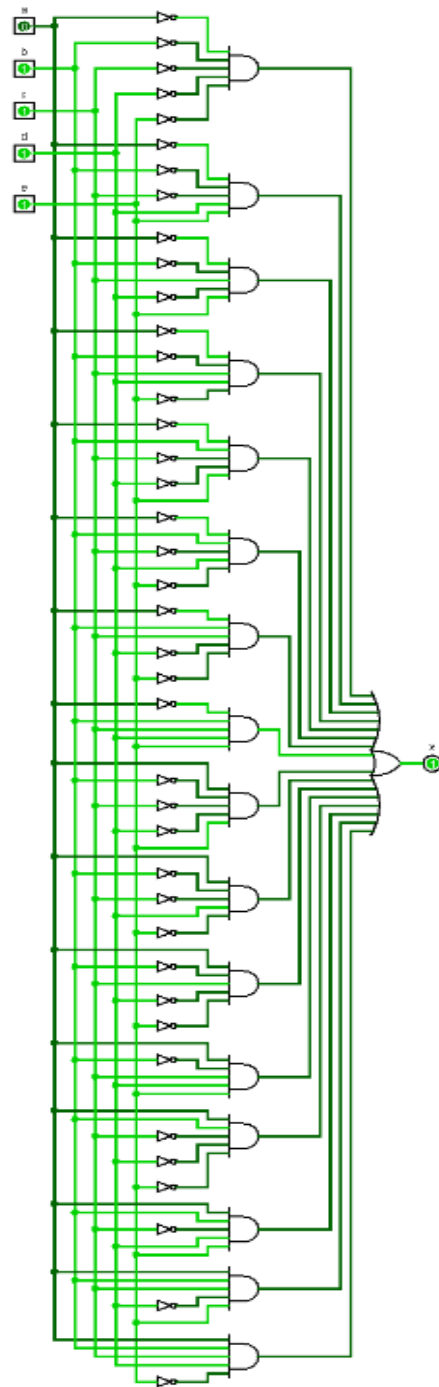**Experimental Analysis:**


- **Circuit Diagram:**

When even number of inputs are 1, the output is 1.



Exp: 3.4.2

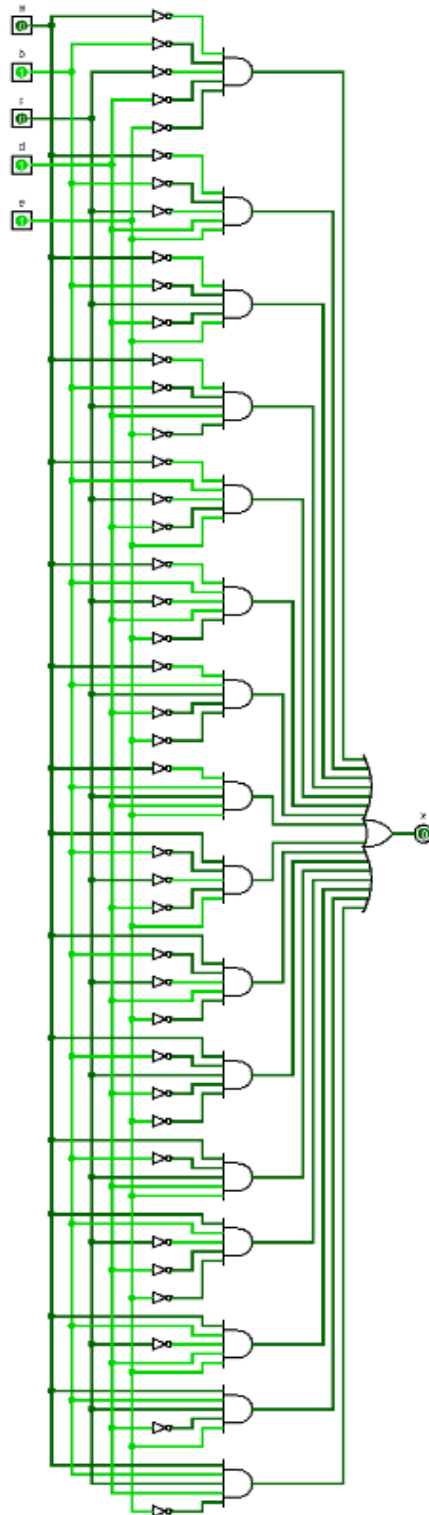When odd number of inputs are 1, the output is 0.



Exp: 3.4.2

- **Truth Table:**

a	b	c	d	e	x
0	0	0	0	0	1
0	0	0	0	1	0
0	0	0	1	0	0
0	0	0	1	1	1
0	0	1	0	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	0	1	1
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	0	1	0
0	1	1	1	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	0	1	1
1	0	0	1	0	1
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	0	1	0
1	0	1	1	0	0
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	0	1	0
1	1	0	1	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	0	1	1
1	1	1	1	0	1
1	1	1	1	1	0

**Conclusion:** In this experiment, we discussed about X-NOR gate operation by giving five inputs. From the truth table, we came to know that a true output results if even number of the inputs to the gate is true. On the other hand, if odd number of inputs are true, a false output results.